

VIET NAM NATIONAL UNIVERSITY HO CHI MINH CITY
HO CHI MINH CITY UNIVERSITY OF TECHNOLOGY
FACULTY OF COMPUTER SCIENCE AND ENGINEERING



SEMESTER 232 - CO3098 - CC02

LSI LOGIC DESIGN
REPORT LABORATORY 1 - BOUND FLASHER

Under the guidance of: Prof. Thien-An Nguyen

Student: Nguyen Van Thanh Dat - 2152055

HO CHI MINH CITY, APRIL 2024



Contents

1	Specification	3
2	Implementation	3
3	Simulation	7

1 Specification

Create RTL code for the Bound Flasher with 16 lamps which has operation as below:

- At the initial state, all lamps are OFF. If the flick signal is ACTIVE (set 1), the flasher starts operating:
 1. The lamps are turned ON gradually from lamp[0] to lamp[5].
 2. The lamps are turned OFF gradually from lamp[5] (max) to lamp[0] (min).
 3. **The lamps are turned ON gradually from lamp[0] to lamp[10].**
 4. The lamps are turned OFF gradually from lamp[10] (max) to lamp[5] (min).
 5. **The lamps are turned ON gradually from lamp[5] to lamp[15].**
 6. The lamps are turned OFF gradually from lamp[15] to lamp[0].
 7. Finally, the lamps are turned ON then OFF simultaneously (blink), and return to the initial state.
- **Additional condition:** At each kickback point (*lamp[5]* and *lamp[10]*), if the flick signal is ACTIVE, the lamps will turn OFF gradually again to the min lamp of the previous state, then continue operation as above description. For simplicity, kickback points are considered only when the lamps are turned ON gradually, except in the first state.

2 Implementation

Based on the given specification, we can utilize some concepts with RTL code to implement the Bound Flasher:

```
1 `timescale 1ns / 1ps
2 //////////////////////////////////////
3 // Company: HCMUT
4 // Engineer: Nguyen Van Thanh Dat
5 //
6 // Create Date: 03/03/2024 02:28:06 PM
7 // Design Name: BoundFlasherLab1
8 // Module Name: BoundFlasher
9 // Project Name: LAB1
10 // Revision: Prof. Nguyen Thien An
11 // Revision 0.01 - File Created
12 //////////////////////////////////////
13
14 module boundFlasher(
15     input clk, flick, rst,
16     output reg [15:0] leds
17 );
18
19     parameter s0 = 0;
20     parameter s1 = 1;
21     parameter s2 = 2;
22     parameter s3 = 3;
```

```
23     parameter s4 = 4;
24     parameter s5 = 5;
25     parameter s6 = 6;
26     parameter s7 = 7;
27
28     parameter timing = 100;
29
30     integer counter = 0;
31
32     reg [2:0] state = s0; /**NOTE: LAB 3. JUST NEED TO CHANGE reg from
33     [3:0] to [2:0], then everything is good
34
35     always @(posedge clk, posedge rst) begin
36         if (rst) begin
37             state <= s0;
38             counter <= 0;
39         end
40
41         else begin
42             case(state)
43                 s0:
44                     begin
45                         leds <= 16'h0000;
46                         if(flick == 0) state <= s0;
47                         else state <= s1;
48                     end
49                 s1:
50                     begin
51                         counter <= counter + 1;
52                         if(counter == timing) begin
53                             leds <= (leds << 1) + 1; //gradually ON
54                             counter <= 0;
55                         end
56                         if (leds == 16'h003F) begin //L[5]
57                             state <= s2;
58                             counter <= 0;
59                         end
60                     end
61                 s2:
62                     begin
63                         counter <= counter + 1;
64                         if (counter == timing) begin
65                             leds <= leds >> 1; //gradually OFF
66                             counter <= 0;
67                         end
68                         if (leds == 16'h0000) begin //-> L[0]
69                             state <= s3;
70                             counter <= 0;
```

```
70         end
71     end
72     s3:
73     begin
74         counter <= counter + 1;
75         if (counter == timing) begin
76             leds <= (leds << 1) + 1; //L[0] -> L[5]* -> L
[10]*
77             counter <= 0;
78         end
79
80         if (leds == 16'h003F) begin
81
82             if(flick == 1) begin
83                 state <= s2;
84                 counter <= 0;
85             end
86         end
87
88         else if (leds == 16'h07FF) begin
89             counter <= 0;
90             if(flick == 1) state <= s2;
91             else state <= s4;
92         end
93     end
94     s4:
95     begin
96         counter <= counter + 1;
97         if(counter==timing) begin
98             leds <= leds >> 1;
99             counter <= 0;
100        end
101        if (leds == 16'h001F) begin // L[5]
102            counter<=0;
103            state <= s5;
104        end
105    end
106
107    s5:
108    begin
109        counter <= counter + 1;
110        if (counter == timing) begin
111            counter <= 0;
112            leds <= (leds << 1) +1; //case, increase to L[5]
and check KBP
113        end
114        if (leds == 16'h003F || leds == 16'h07FF) begin
115            if (flick == 1) begin
```

```
116         counter <=0;
117         state <= s4;
118     end
119 end
120 if (leds == 16'hFFFF && flick == 0) begin
121     counter <=0;
122     state <= s6;
123 end
124 end
125
126 s6:
127     begin
128         counter <= counter + 1;
129         if (counter == timing) begin
130             counter <= 0;
131             leds <= leds >> 1; //OFF to L[0]
132         end
133         if(leds == 16'h0000) begin
134             counter <= 0;
135             state <= s7;
136         end
137     end
138 s7:
139     begin //ON and OFF SIMULTANEOUSLY
140         leds <= 16'hFFFF;
141         counter <= counter + 1;
142         if (counter == timing) begin
143             counter <= 0;
144             state <= s0;
145         end
146     end
147 end
148 endcase
149 end
150 end
151 endmodule
```

3 Simulation

Here is the test bench file for the Bound Flasher for further simulation:

```
1 module boundFlasher_tb;
2     reg clk;
3     reg flick;
4     reg rst;
5     wire [15:0] leds;
6
7     boundFlasher UUT
8     (
9         clk, flick, rst, leds
10    );
11
12    // Create clock
13    always #1 clk = !clk;
14
15    initial begin
16        // Initial state
17        clk = 0;
18        flick = 0;
19        rst = 0;
20        #10;
21        flick = 1;
22        @(UUT.state == 2) rst = 1;
23        #20
24        // flick = 1 -> system starts operating
25        rst=0;
26        flick = 1;
27        #10;
28        flick = 0;
29
30        // Test kickback points at L[5] at state 3
31        @(UUT.state == 3)
32            begin
33                #10;
34                flick = 1;
35            end
36        // Set flick = 1 to transit to next state
37        @(UUT.state == 2) flick = 0;
38        // Test kickback points at L[10] at state 3
39        @(UUT.leds == 16'h007F) flick=1;
40        @(UUT.state == 2) flick = 0;
41
42
43        // Test kickback points at L[5] at state 5
44        @(UUT.state == 5) flick = 1;
```

```

45    @(UUT.state == 4) flick = 0;
46    // Test kickback points at L[10] at state 5
47    @(UUT.leds == 16'h007F) flick=1;
48    @(UUT.state == 4) flick = 0;
49    #50000;
50    $finish;
51 end
52
53 initial begin
54     $recordfile ("waves");
55     $recordvars ("depth=0", boundFlasher_tb);
56 end
57
58 endmodule

```

In the beginning, it is immediately evident that the system will not operate in case there is no flick signal. Then, we activate the flick signal in order to make the Bound Flasher start operating:

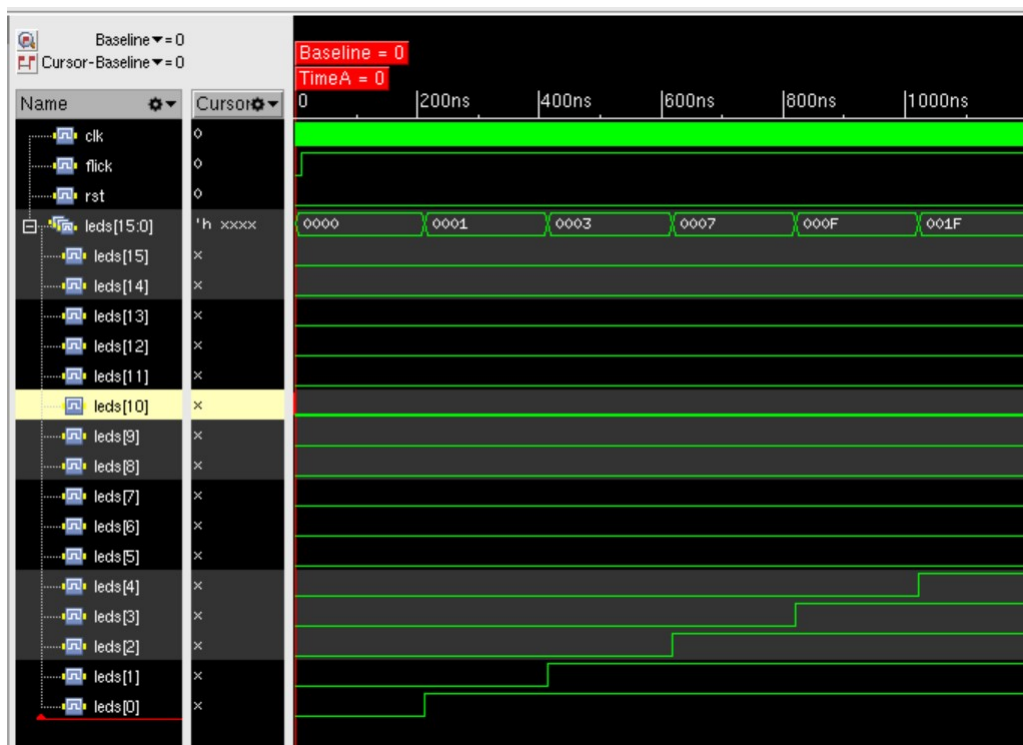


Figure 1: Flick signal case

Moving on to the reset (rst), this will make the system reset straight away whenever users activate the reset function:

 


Figure 2: Reset case

Upon to the given specification mentioned initially, we will simulate to check the state of the LEDs in kickback points with active flick signal (LEDs[5] and LEDs[10] in the situations where the lamps are turned ON gradually from lamp[0] to lamp[10] and the lamps are turned ON gradually from lamp[5] to lamp[15]) and also the system runs without active flick signal when encountering kickback points as mentioned:

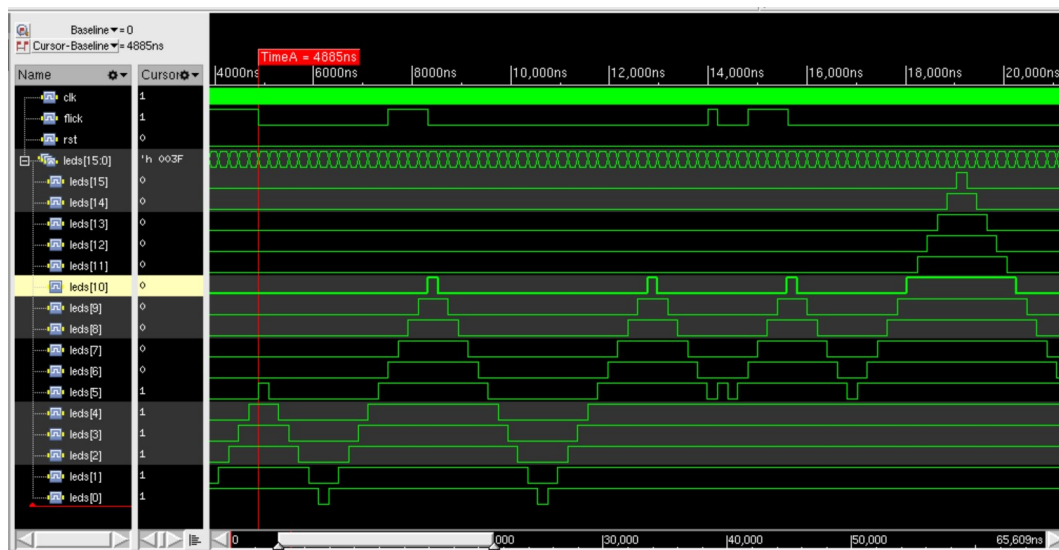


Figure 3: Final simulation